
Nama : Danang Ady Saputro Widodo

NIM : L200180205

Kelas : G

Nomor 1

A.

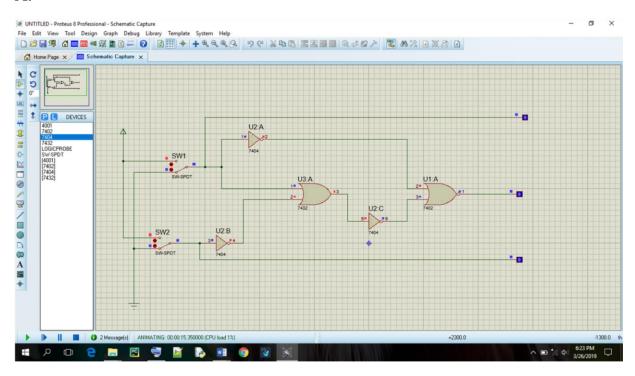

B.Fungsi bolean 
$$(\overline{Y+X}) + X = (Y+X)+X$$

## C. Tabel kebeneran

X	Y	L1	L2	Z
0	0	0	0	0
1	0	1	0	1
0	1	0	1	0
1	1	1	1	1

## Diagram Waktu

X				
	0	1	0	1
Y				
	0	0	1	1
Z				
	0	1	0	1

## Nomor 2

